



**Faculty of Engineering and Technology
Electrical and Computer Engineering Department**

**Computer Architecture
ENCS4370**

Project 2 Report

Prepared by:

Osaid Nur	1210733
Moath Wajeeh	1210125
Obayda Sarraj	1211128

Instructor: Dr. Aziz Qaroush
Section: 3
Date: 19/6/2024

Abstract

This project focuses on the design and verification of a simple multicycle RISC processor with a 16-bit instruction and word size. The processor architecture includes eight 16-bit general-purpose registers and separate instruction and data memories. It supports various instructions, including arithmetic, branch, and jump operations. The report details the architectural design, implementation, and verification processes, emphasizing the Datapath and control signals. This approach demonstrates the successful creation of a functional multicycle RISC processor.

Table of Contents

Abstract	I
Table of Contents	II
Table of Figures:.....	III
List of Tables:.....	IV
1. Design Specifications	1
1.1 Overview	1
1.2 Instruction Formats:.....	1
1.2.1 R-Type:.....	1
1.2.2 I-Type:	1
1.2.3 J-Type:.....	2
1.2.4 S-Type:	2
1.3 Instruction Set:	3
2. Components of Datapath.....	4
2.1 Multiplexer:	4
2.2 Instruction Memory	5
2.3 Data Memory	5
2.4 Register File	7
2.5 Arithmetic Logic Unit (ALU) :	8
3. Control Path	9
3.1 Control Unit truth table.....	9
3.2 Logic equation of the control signals	10
4. State Diagram	11
5. Project Data Path	12
6. Simulation and Testing results	13
Conclusion:	15

Table of Figures:

Figure 1. R-type instruction format	1
Figure 2. I-type instruction format	1
Figure 3. J-Type instruction format for jump and call instructions	2
Figure 4. J-Type instruction format for “ret” instruction.....	2
Figure 5. S-Type instruction format.....	2
Figure 6. Mux 4x1 used in Datapath.....	4
Figure 7. Instruction memory	5
Figure 8. Data Memory.....	6
Figure 9. Register File	7
Figure 10. ALU	8
Figure 11: State Diagram	11
Figure 12: Instructions set	13
Figure 13: wave form.....	13
Figure 14: Another testbench waveform.....	14
Figure 15: another waveform	14

List of Tables:

Table1 Control Signal Truth Table	9
Table2 Boolean Equation Table	10

1. Design Specifications

1.1 Overview

This project implements a MIPS architecture processor within the RISC architecture family. The processor supports a defined set of instructions and includes the following features:

- 1- Each instruction in the set is 32 bits in length.
- 2- The design includes 16 32-bit general-purpose registers, labeled from R0 to R15.
- 3- Program Counter (PC) is a 32-bit special-purpose register.
- 4- stack pointer (SP) is 32-bit special purpose register.
- 5- four distinct instruction types – R-type, I-type, J-type, and S-type.
- 6- The processor is designed with two separate physical memory units: one for storing instructions and the other for data.
- 7- Arithmetic Logic Unit is also used to decide the outcomes of certain instructions, like whether to take a branch or not.

1.2 Instruction Formats:

The instruction set has the following instructions formats:

1.2.1 R-Type:

 


Figure 1. R-type instruction format

Opcode (4 bits): specifies the operation type for the processor.

Rd (3 bits): Destination register (the result will be stored in this register)

Rs1 (3 bits): first source register

Rs2 (3 bits): second source register

Unused (3 bits)

1.2.2 I-Type:

 


Figure 2. I-type instruction format

Opcode (4 bits): specifies the operation type for the processor.

Rd (3 bits): Destination register (the result will be stored in this register)

Rs1 (3 bits): first source register

Immediate (5 bits): unsigned for logic instructions and signed otherwise

m (1 bit): this is for **load** and **branch** instructions, such that:

For the load : **0** : LBs load byte with zero extension
 1 : LBU load byte with sign extension

For the branch : **0** : compare Rd with Rs1

1 : compare Rd with R0

1.2.3 J-Type:

This type includes two instruction formats. The following is the instruction format for **Jump** and **call** instructions :

 


Figure 3. J-Type instruction format for jump and call instructions

Opcode (4 bits): specifies the operation type for the processor.

Jump Offset (12 bits): Specifies the offset relative to the current program counter (PC) value. the target address is calculated by concatenating the most significant 7-bit of the current PC with the 12-bit offset after multiplying offset by 2.

New PC = Current PC + 2* jump offset

This represents the instruction format for **ret**:

 


Figure 4. J-Type instruction format for “ret” instruction

Opcode (4 bits): specifies the operation type for the processor.

Unused (12 bits): because in the 'ret' instruction, only the value in R7 is moved to the PC so these bits are not needed.

1.2.4 S-Type:

This format support only one instruction as following:

Sv rs, imm # M[rs] = imm

 


Figure 5. S-Type instruction format

1.3 Instruction Set:

No.	Instruction	Format	Meaning	opcode	m bit
1	AND	R-Type	$\text{Reg(Rd)} = \text{Reg(Rs1)} \& \text{Reg(Rs2)}$	0000	
2	ADD	R-Type	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Reg(Rs2)}$	0001	
3	SUB	R-Type	$\text{Reg(Rd)} = \text{Reg(Rs1)} - \text{Reg(Rs2)}$	0010	
4	ADDI	I-Type	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Imm}$	0011	
5	ANDI	I-Type	$\text{Reg(Rd)} = \text{Reg(Rs1)} + \text{Imm}$	0100	
6	LW	I-Type	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm})$	0101	
7	LBu	I-Type	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm})$	0110	0
8	LBs	I-Type	$\text{Reg(Rd)} = \text{Mem}(\text{Reg(Rs1)} + \text{Imm})$	0110	1
9	SW	I-Type	$\text{Mem}(\text{Reg(Rs1)} + \text{Imm}) = \text{Reg(Rd)}$	0111	
10	BGT	I-Type	if ($\text{Reg(Rd)} > \text{Reg(Rs1)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1000	0
11	BGTZ	I-Type	if ($\text{Reg(Rd)} > \text{Reg(0)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1000	1
12	BLT	I-Type	if ($\text{Reg(Rd)} < \text{Reg(Rs1)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1001	0
13	BLTZ	I-Type	if ($\text{Reg(Rd)} < \text{Reg(R0)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1001	1
14	BEQ	I-Type	if ($\text{Reg(Rd)} == \text{Reg(Rs1)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1010	0
15	BEQZ	I-Type	if ($\text{Reg(Rd)} == \text{Reg(R0)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1010	1
16	BNE	I-Type	if ($\text{Reg(Rd)} != \text{Reg(Rs1)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1011	0
17	BNEZ	I-Type	if ($\text{Reg(Rd)} != \text{Reg(Rs1)}$) Next PC = PC + sign_extended (Imm) else PC = PC + 2	1011	1
18	JMP	J-Type	Next PC = {PC[15:10], Immediate}	1100	
19	CALL	J-Type	Next PC = {PC[15:10], Immediate} PC + 4 is saved on r15	1101	
20	RET	J-Type	Next PC = r7	1110	
21	Sv	S-Type	$\text{M[rs]} = \text{imm}$	1111	

2. Components of Datapath

To implement the processor design, several key components are required. We will now provide a detailed description of these essential components.

2.1 Multiplexer:

A multiplexer, often abbreviated as MUX, is a combinational circuit that selects one of many input signals and forwards the selected input to a single output line. The selection of the input line is controlled by a set of selection lines.

In the Datapath, we used various MUXes. This is an example of a MUX used in the Datapath.

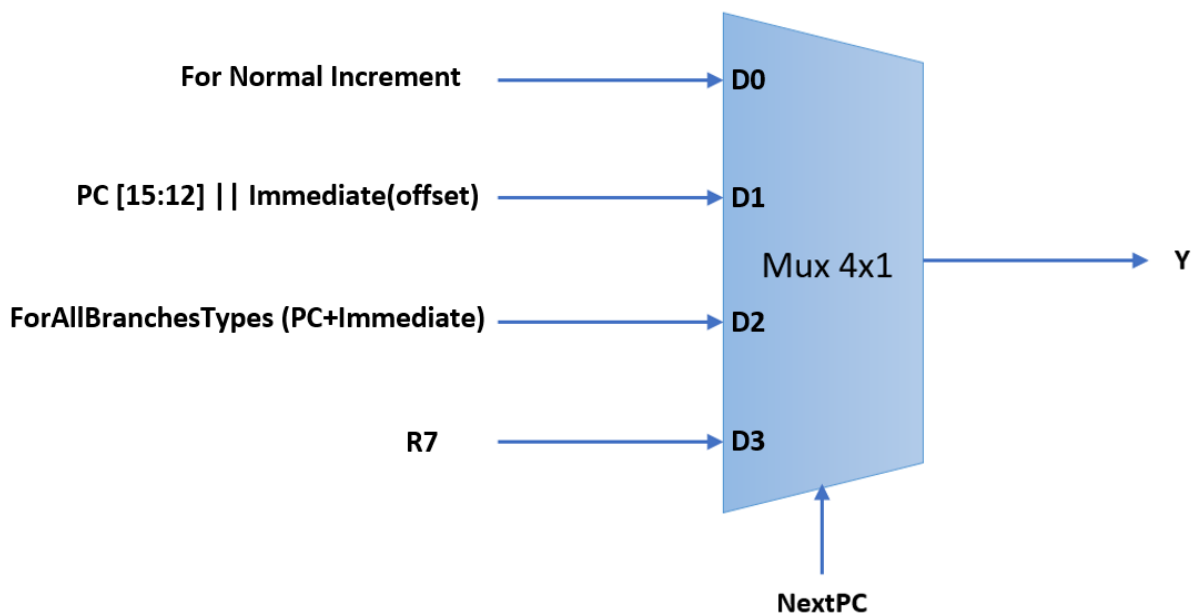


Figure 6. Mux 4x1 used in Datapath

This MUX, located at the leftmost part of the Datapath, determines the PC value based on the instruction:

If (**NextPC** = **00**) , the new PC value is $PC + 2$, which is used in most instructions

If (**NextPC** = **01**) , The new PC value is the result of concatenating the current PC value with Immediate. This is used in jump instructions.

If (**NextPC** = **10**) , The new value of PC is equal to old PC value + Immediate , This used in the branches instructions .

If (**NextPC** = **11**), the new PC value is the value stored in R7, which contains the saved address after a function call. This is used in the "ret" instruction.

2.2 Instruction Memory

Instruction memory is a vital component of a computer's architecture. It stores the instructions that the processor needs to execute. In our design, the instruction memory is separate from the data memory, allowing for more efficient access and execution of instructions. This memory is read-only during program execution, ensuring the instructions remain unchanged. When the processor fetches an instruction, it uses the program counter (PC) to access the correct memory location.

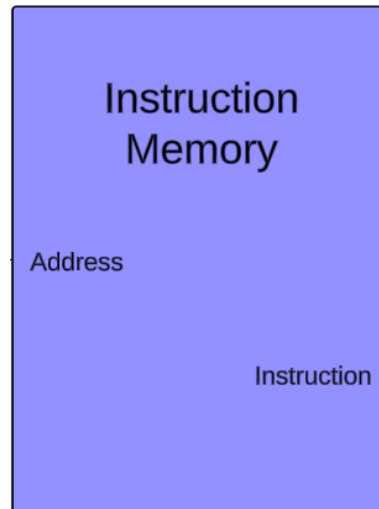


Figure 7. Instruction memory

As shown, the instruction memory has one input, the address, and one output, the 16-bit instruction stored at that address.

2.3 Data Memory

The other part of memory in our design is Data memory. It stores the data that the processor needs to read from or write to during program execution. This memory is byte-addressable, allowing each byte to have a unique address for efficient access. The processor interacts with data memory through addresses, enabling it to read or write 16-bit data values. Data memory is used for storing variables, intermediate results, and other data required by the program. In the design, it's important to ensure that data memory operations are synchronized with the processor to maintain data integrity and performance.

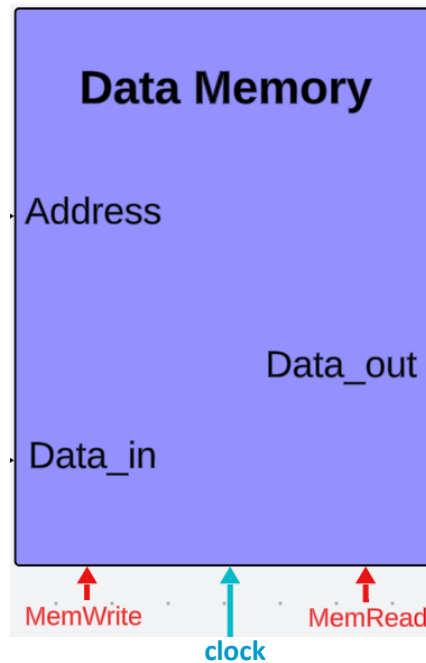


Figure 8. Data Memory

As shown in the above image , Data memory has the following inputs and outputs :

Input :

Address: This specifies the exact location in the memory where data will be stored or from where it will be retrieved. Each memory location has a unique address.

Data_in: This input carries the actual information or data that you want to store in the memory.

Clock: The clock signal synchronizes operations within the memory. It ensures that data is written to or read from the correct memory location at the appropriate time.

MemRead : enables the read operation in the memory .

MemWrite : enables the write operation in the memory .

Output:

Data_out: provides the data retrieved from the specified memory address, serving as the result of a read operation.

2.4 Register File

A register file is a critical component in computer processors designed to store temporary data for fast access. It consists of multiple registers, each functioning like a small storage unit with its unique address. These registers hold essential data required by the CPU for immediate processing tasks, including numbers, memory addresses, and control signals. Unlike dynamic RAM (DRAM) used in main memory, register files typically use static RAM (SRAM), enabling faster access speeds. In our project, we have 8 registers, each capable of storing data up to 16 bits wide.

 


Figure 9. Register File

As shown , the Register file has the following inputs and outputs :

Input:

RA (Register Address A): Specifies the register address to read data from and send to BusA.

RB (Register Address B): Specifies the register address to read data from and send to BusB.

RW (Register Write): Specifies the register address to write data to from BusW.

RegWrite: Control signal to enable or disable writing to the register specified by RW.

Output :

BusA: carries the data read from the register specified by RA.

BusB: carries the data read from the register specified by RB.

BusW: carries data to be written into the register specified by RW if the RegWrite signal is active.

2.5 Arithmetic Logic Unit (ALU) :

The ALU, or Arithmetic Logic Unit, is a crucial part of the computer's central processing unit (CPU). It performs all arithmetic and logical operations. For example, it can add, subtract, multiply, and divide numbers. It also handles logical operations like AND, OR, and NOT. The ALU takes input data from the registers, processes it, and then sends the result back to the registers or memory. It operates under the control of the CPU's instruction set.

 


Figure 10. ALU

As shown , the ALU has the following inputs and outputs :

Inputs:

Two operands (A and B): These are 16-bit numbers.

Opcode: Determines the operation to be executed .

Outputs:

status flags: such as zero, carry, and overflow, which provide information about the outcome of the operation .

Result : This is where the ALU stores the outcome of the operation performed on the inputs A and B.

3. Control Path

3.1 Control Unit truth table

1 Control Signal Truth Table Table

Inst.	NextPc	ExtMode	SecondOp	writeDes	RegWrite	ALUSrc	ALUOp	MemoryIn	DataAddress	MemRead	MemWrite	WriteData
AND	0	X	0	0	1	0	0	X	0	0	0	0
ADD	0	X	0	0	1	0	1	X	0	0	0	0
SUB	0	X	0	0	1	0	2	X	0	0	0	0
ADDI	0	1	X	0	1	1	1	X	0	0	0	0
ANDI	0	0	X	0	1	1	0	X	0	0	0	0
LW	0	1	X	0	1	1	1	1	0	1	0	1
LBu	0	0	X	0	1	1	1	1	0	1	0	1
LBs	0	1	X	0	1	1	1	1	0	1	0	1
SW	0	X	X	X	0	1	1	1	0	0	1	X
BGT	2	1	0	X	X	1	2	X	X	0	0	X
BGT	0	1	0	X	X	1	2	X	X	0	0	X
BGTZ	2	1	1	X	X	1	2	X	X	0	0	X
BGTZ	0	1	1	X	X	1	2	X	X	0	0	X
BLT	2	1	0	X	X	1	2	X	X	0	0	X
BLT	0	1	0	X	X	1	2	X	X	0	0	X
BLTZ	2	1	1	X	X	1	2	X	X	0	0	X
BLTZ	0	1	1	X	X	1	2	X	X	0	0	X
BEQ	2	1	0	X	X	1	2	X	X	0	0	X
BEQ	0	1	0	X	X	1	2	X	X	0	0	X
BEQZ	2	1	1	X	X	1	2	X	X	0	0	X
BEQZ	0	1	1	X	X	1	2	X	X	0	0	X
BNE	2	1	0	X	X	1	2	X	X	0	0	X
BNE	0	1	0	X	X	1	2	X	X	0	0	X
BNEZ	2	1	1	X	X	1	2	X	X	0	0	X
BNEZ	0	1	1	X	X	1	2	X	X	0	0	X
JMP	1	X	X	X	X	X	X	X	X	0	0	X
CALL	1	X	X	1	1	X	X	X	X	0	0	2
RET	3	X	2	X	X	X	X	X	X	0	0	X
Sv	1	X	X	X	0	X	X	0	1	0	1	X

3.2 Logic equation of the control signals

2 Boolean Equation Table Table

Signal	Boolean Equation
NextPc	(BGT BGTZ BLT BLTZ BEQ BEQZ BNE BNEZ) 2 & JMP & CALL & RET
ExtMode	ADDI LW LBs BLT BLTZ BEQ BEQZ BNE BNEZ
SecondOp	BGT BGTZ BLT BLTZ BEQ BEQZ BNE BNEZ
writeDes	CALL
RegWrite	AND ADD SUB ADDI ANDI LW LBU LBs CALL
ALUSrc	ADDI ANDI LW LBU LBs SW
ALUOp [1]	ADD SUB ADDI LW LBU LBs SW
ALUOp [2]	AND ADD ANDI LW LBU LBs SW
MemoryIn	LW LBU LBs SW
DataAddress	Sv
MemRead	LW LBU LBs
MemWrite	SW Sv
WriteData	CALL (LW LBU LBs 1)

4. State Diagram


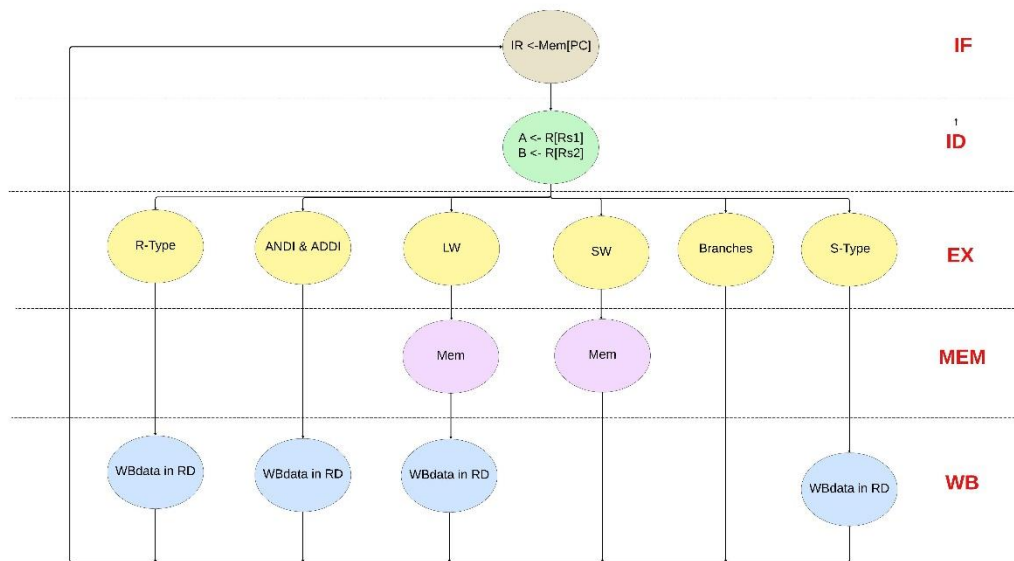


Figure 11: State Diagram

5. Project Data Path

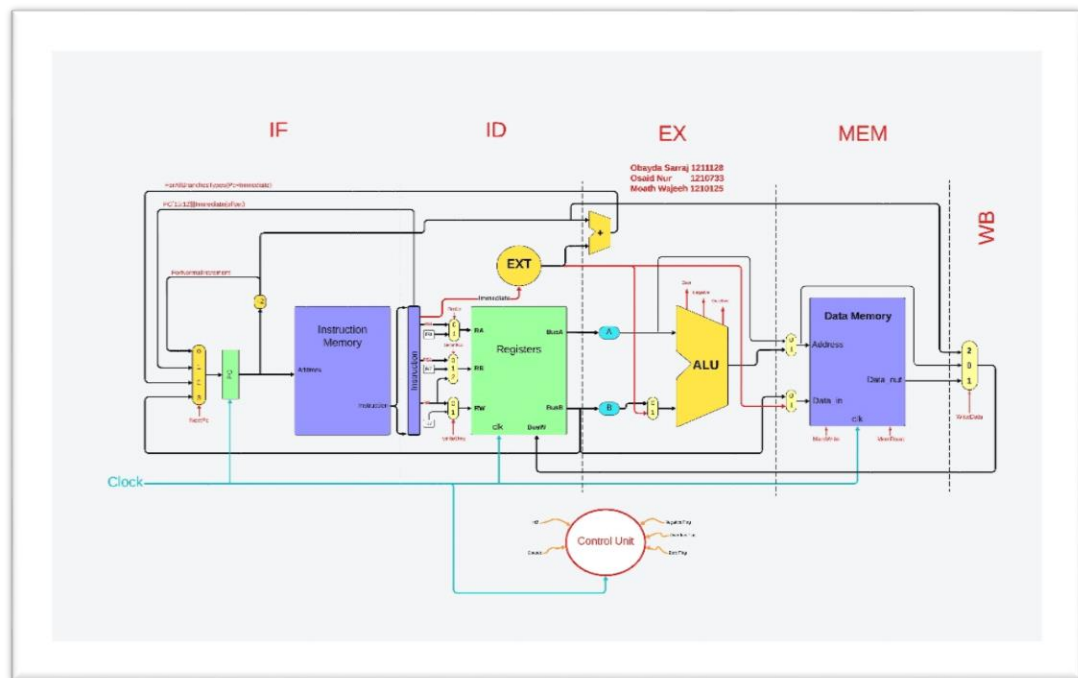

6. Simulation and Testing results

```
instruction_memory[0] = 16'b0;
instruction_memory[2] = 16'b0;
instruction_memory[4] = { BLT, 1'b0 ,R4, R4, 5'b00001 };
instruction_memory[5] = { ADD, 1'b1 ,R6, R0, 5'b0001 };
instruction_memory[6] = { BGT, 1'b0 ,R2, R1, 5'b00001 };
instruction_memory[7] = { ADD, 1'b1 ,R6, R4, 5'b00010 };
instruction_memory[9] = { BEQ, 1'b0 ,R1, R3, 5'b00011 };
instruction_memory[12] = { AND, 1'b1 ,R6, R1, 5'b00001 };
instruction_memory[13] = { BNE, 1'b0 ,R1, R1, 5'b00001 };
instruction_memory[15] = { BNEZ, 1'b1 ,R6, R4, 5'b11110 };
```

Figure 12: Instructions set

These instructions that we have tested our program with.

Also, we have attached some testbenches for Data memory and register file, we tested them also.

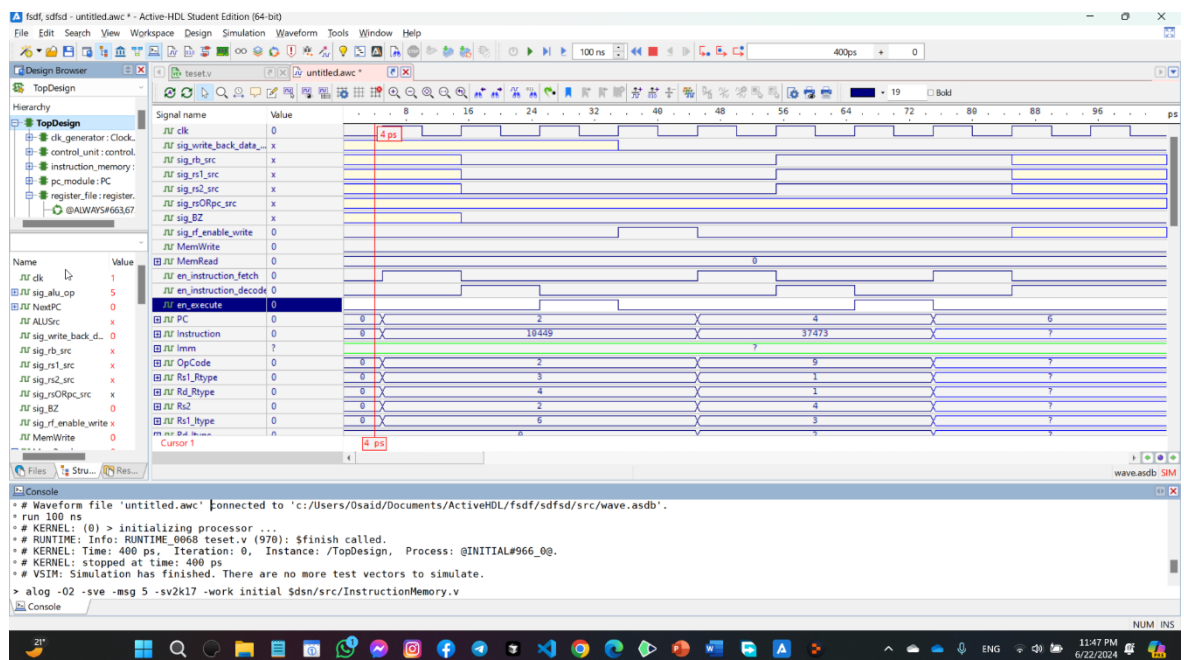


Figure 13: wave form

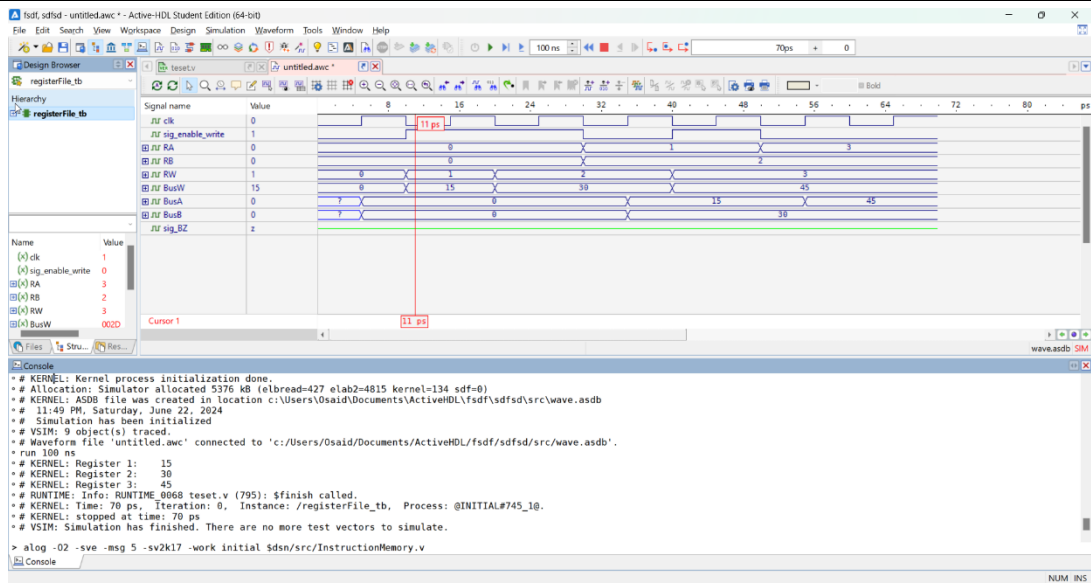


Figure 14: Another testbench waveform

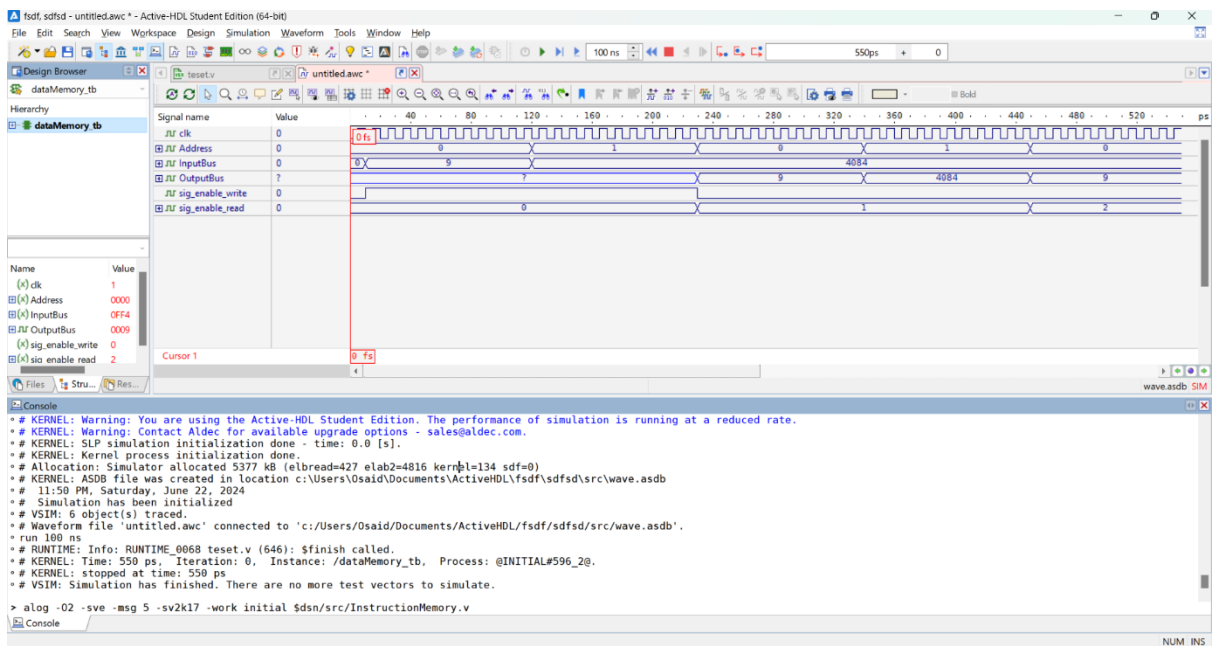


Figure 15: another waveform

Conclusion:

Building and testing a multi-cycle RISC processor using Verilog has taught us a lot about how computers are built and how digital logic works. Using a multi-cycle model helped us use resources efficiently and make the control system simpler, while still handling a wide range of operations like moving data, jumping to different parts of code, and storing information. We tested the processor thoroughly to make sure it worked correctly with the instructions we wanted it to follow. This project showed how we can apply concepts from digital logic and computer organization in a Verilog-based environment, giving us a solid base for exploring more about processor design and hardware description languages. It also helped us understand the key parts and considerations needed to develop computer processors.